

C10T ELECTRONICS


OPAMP

for 4TH SEM.

- The Last class - Log amplifier & Anti log amplifier. (then-1)
- ii) CMRR, Slew Rate, Frequency Response of the OPAMP

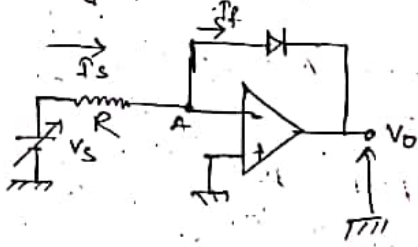8. Log Amplifier :

for OPAMP log Amplifier o/p is proportional to the Log of the i/p voltage.



Since, there is a virtual ground at the point A, so same current passes through R and diode,

$$I_s = I_f$$

$$\Rightarrow \frac{V_s - 0}{R} = I_0 \left(e^{\frac{eV}{\eta KT}} - 1 \right)$$

$$\approx I_0 e^{\frac{eV}{\eta KT}}$$

$$\text{or, } V_o = -V_f = -\frac{\eta KT}{e} \ln \frac{V_s}{I_0 R}$$


• I_0 = reverse saturation current.

$\eta = 1$ for Ge diode.

$= 2$ for Si


output $\propto \log(\text{input})$. This device working within wide range of i/p voltages.

Antilog Amplifier :

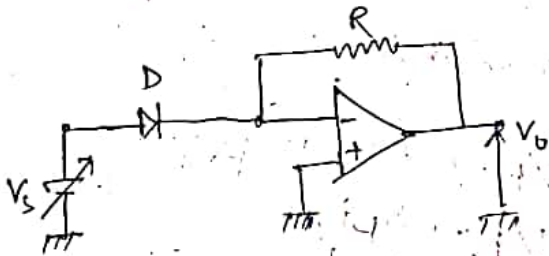

In log amplifier with we re arranged R and D position, we can get antilog Amplifier.

9. voltage Comparator :

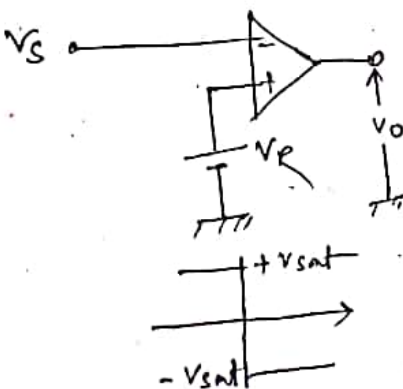


voltage comparator can compare two voltages. OPAMP comparators can compare i/p signal V_s with a reference voltage V_R .
* As, $V_s < V_R$, o/p $\rightarrow V_o$ goes to maximum positive saturation $+V_{sat}$.

as V_s cross V_R i.e. $V_s > V_R$, the OPAMP o/p switches to the negative saturation value ($-V_{sat}$). Thus by looking at the output voltages we can instantly identify whether the voltage V_s is greater than or less than V_R .

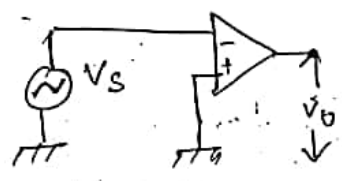
10.

Zero-Crossing detector

The comparator can be used to generate a symmetric square waves form sine waves by just taking $V_R = 0$ and choosing V_s as a sinusoidal voltage



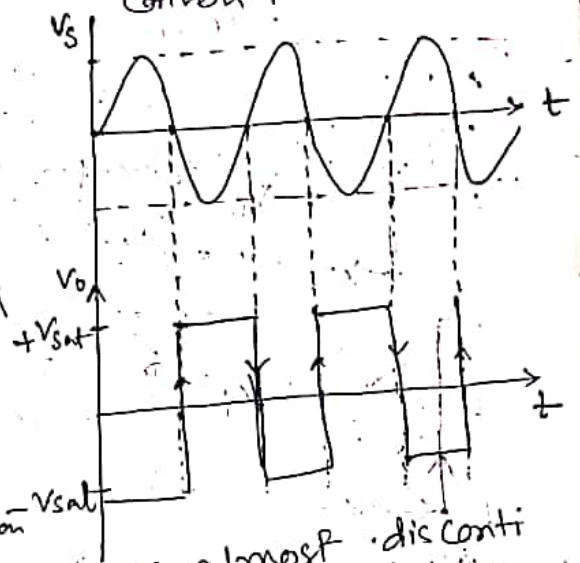Zero crossing detector
Convert $\sin \rightarrow \square \square$



- when V_s passes through the +ve values the V_o is driven into the negative saturation, $-V_{sat}$, when V_s passes through '0' towards negative values the output V_o is driven to positive saturation $+V_{sat}$. Thus if $V_R = 0$, the o/p changes almost discontinuously from one state to the other every time the input signal passes through zero. For this such a configuration is called a zero crossing detector.
- it is also used to convert a sinusoidal waveform into a square waveform.


Maximum value = $+V_{sat}$

Minimum " = $-V_{sat}$

19


19

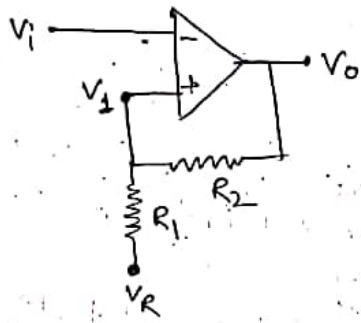11. Schmitt trigger: A comparator uses positive or regenerative feedback and exhibits the phenomenon of hysteresis called a regenerative comparator or Schmitt trigger.



• Schmitt trigger using OPAMP
 V_R = Reference voltage.
 V_i = input voltage.

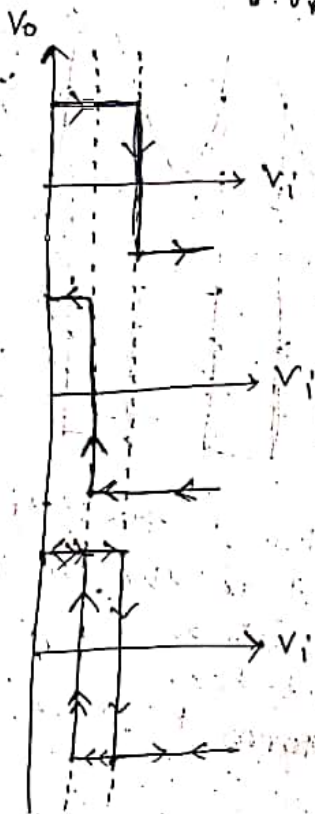- V_i → applied inverting terminal
- V_R → " " Non "



transfer characteristics for increasing V_i

transfer characteristics for decreasing V_i

Complete transfer characteristics showing hysteresis.

• • When, $V_i < V_1$ the output V_o goes to the positive saturation level $+V_{sat}$. then using super-position principle we get;

$$V_i = \frac{R_2 V_R}{R_1 + R_2} + \frac{R_1 V_{sat}}{R_1 + R_2} \geq V_1 \text{ (Say)}$$

→ V_i now increased but $V_o = \text{const}$ at $+V_{sat}$ until $V_i = V_1$, $V_i \geq V_1$

• • At critical or threshold, critical or triggering voltage, the o/p regeneratively switches to $V_o = -V_{sat}$

... $V_0 = -V_{sat}$ and remains at that value until $v_i > V_1$, the voltage at the non-inverting terminal. For $v_i > V_1$ is given by,

$$V_1 = \frac{R_2 V_e}{R_1 + R_2} - \frac{R_1 V_{sat}}{R_1 + R_2} = V_2 \text{ (Say)}$$


• If the voltage v_i is now decreased the o/p remains at $-V_{sat}$ (and $v_i = V_2$), at this voltage o/p regeneratively switches to $+V_{sat}$.

So, the ckt triggers at different voltages depending on whether the signal is increasing or decreasing, the ckt exhibits hysteresis. Two I/P voltages at which the o/p voltages are changed called trip points.

V_1 is the upper trip points (UTP)
 V_2 is the Lower " (LTP)
 - The difference between two trip points are called hysteresis - V_H . So,


$$V_H = V_1 - V_2 = \frac{2R_1}{R_1 + R_2} \cdot V_{sat}$$

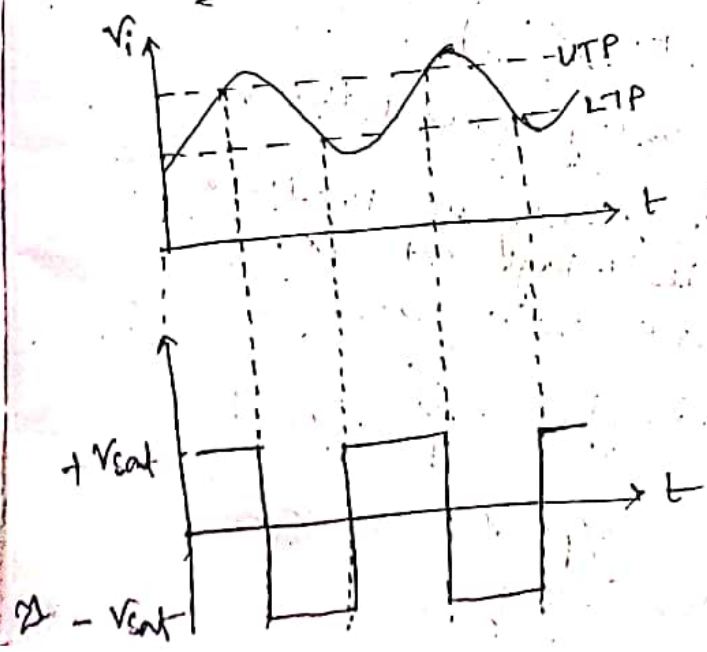⇒ Schmitt trigger produces asymmetric square wave forms from an arbitrary input signal.



- Schmitt trigger have remain of its two stable states indefinitely. It changes its state when a triggering signal is applied, thus this Schmitt trigger circuit also known as the bistable Multivibrator.

Wien bridge Oscillator using OPAMP :

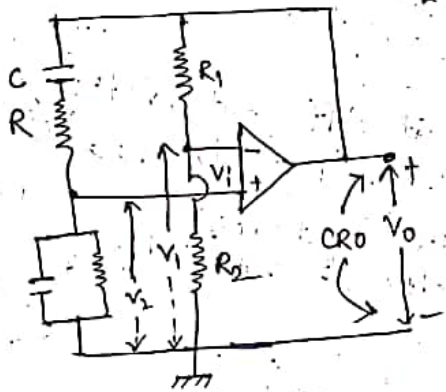

2 RC combination and the resistor R_1 and R_2 forms four arms of the Wien bridge.

- It is a RC oscillator mainly used to produce AF signal.
- phase shift = $360^\circ / 0^\circ$
- Barkhausen criterion valid $\beta A = 1$

$$\text{Now, } V_2 = \frac{V_0}{\left(R + \frac{1}{j\omega C}\right) + \frac{R \cdot \frac{1}{j\omega C}}{\left(R + \frac{1}{j\omega C}\right)}} \times \frac{R \cdot \frac{1}{j\omega C}}{\left(R + \frac{1}{j\omega C}\right)}$$

$$\text{or, } \frac{V_2}{V_0} = \frac{R / (1 + j\omega CR)}{\frac{1 + j\omega CR}{j\omega C} + \frac{R}{1 + j\omega CR}}$$

$$\Rightarrow \text{or, } \frac{V_2}{V_0} = 1 + \frac{(1 + j\omega CR)^2}{j\omega CR} = 3 + j(\omega CR - 1/\omega CR)$$

So, V_2 may lead over or lag behind the V_0

depending on the frequency ω , produce RC combinationable lead-lag network, V_2 will be the phase with V_0 at a freq. given by ω

$$\Rightarrow \omega CR = \frac{1}{\omega CR} \Rightarrow \omega = \frac{1}{CR} \Rightarrow f = \frac{1}{2\pi CR}$$

Now, $\frac{V_2}{V_0} = \frac{1}{3}$ So, $\frac{1}{3}$ of the O/P, feedback to the input.

$$V_1 = \frac{V_0 \cdot R_2}{R_1 + R_2}$$

$$V_i = V_2 - V_1$$

Now, if the bridge is balanced $V_i = 0$.
 $V_1 = V_2$ then,

$$\frac{V_1}{V_0} = \frac{V_2}{V_0} = \frac{1}{3}$$

Now, for $V_i \neq 0$, $\frac{V_1}{V_0} = \frac{R_2}{R_1 + R_2} = \frac{1}{3} - \frac{1}{8}$


[8 is a no. greater than 3]

So, the feedback ratio; $\beta = \frac{V_i}{V_0} = \frac{V_2 - V_1}{V_0} = \frac{1}{8}$

Resistive Network :

• Digital to Analog Converter :

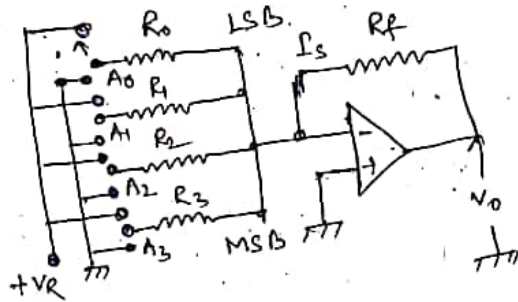A device that produces an analog output voltage from a given or given digital input is called a digital to analog [D/A] converter.



• Weighted Resistor D/A
 net diagram for a four bit parallel D/A converter, which convert a 4 bit parallel digit

word $A_3A_2A_1A_0$ to an analog voltage proportional to the binary number represented by the digit word. When any one of the digit is i.e. '1' is connected to the V_R , when '0' is connected to the ground. the resistance's chosen as,

$$\left\{ \begin{array}{l} R_0 = \frac{R}{2^0} = R \\ R_1 = \frac{R}{2^1} = \frac{R}{2} \\ R_2 = \frac{R}{2^2} = \frac{R}{4} \\ R_3 = \frac{R}{2^3} = \frac{R}{8} \end{array} \right.$$

R can be choose according to the impedance level of the network

$$\begin{aligned} V_0 &= -R_f \cdot I_s \\ &= -R_f \left[\frac{V_R}{R_3} A_3 + \frac{V_R}{R_2} A_2 + \frac{V_R}{R_1} A_1 + \frac{V_R}{R_0} A_0 \right] \\ &= -\frac{V_R R_f}{R} \left[2^3 A_3 + 2^2 A_2 + 2^1 A_1 + 2^0 A_0 \right] \end{aligned}$$

--- $A_i \geq L$ V_R connected
 2.0 '0' Gnd "


So, the o/p is proportional to the numerical value of the binary No. $A_3 A_2 A_1 A_0$. ~~to the numerical decimal value~~

The 4 bit converter can be easily extended to more bits simply by adding more weighted resistors.

disadvantage:

- i) fabricate such amount of Resistors within precision in IC form is problematic.
- ii) value drifted with changing temperature.

© R-2R Ladder D/A Converter:

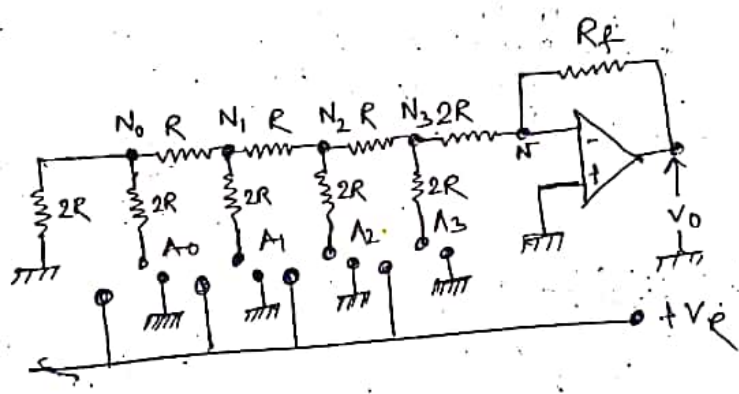

$$V_o = - \frac{R_f}{3R} \frac{V_R}{2^4} [2^3 A_3 + 2^2 A_2 + 2^1 A_1 + 2^0 A_0]$$

To explain the operation of the circuit let all the switches are connected to the ground except A_0 . The resulting resistive portion of the circuit is calculated by applying the Thevenin theory to the left of the Node. thus the circuit becomes simplified.






Apply Thevenin theory to left of the nodes N_1, N_2, N_3
 The equivalent voltage form $V_R/16$ in series with $3R$

if we connect A_0 to V_R , all other to zero.


for next node $V_R/8$, in series with $3R$, $A_1 \rightarrow V_R$

then $V_R/4$ " " $3R$ $A_2 \rightarrow V_R$

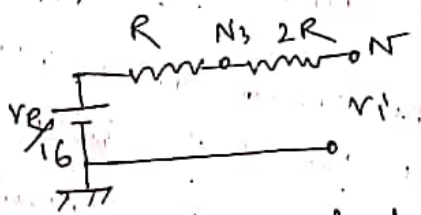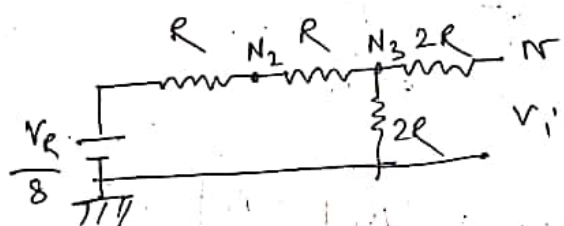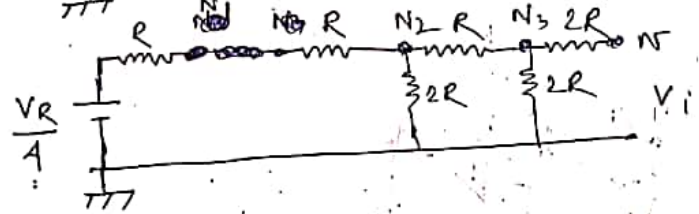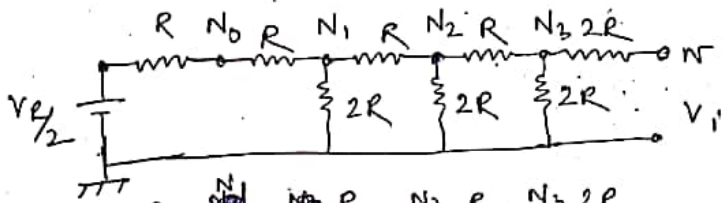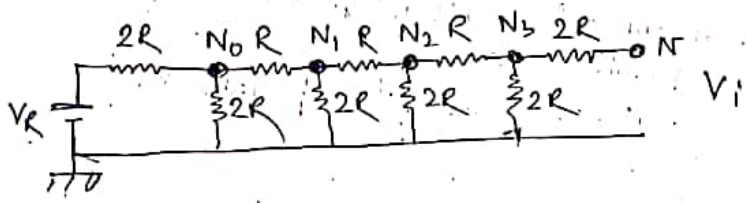" " $V_R/2$ " " $3R$ $A_3 \rightarrow V_R$



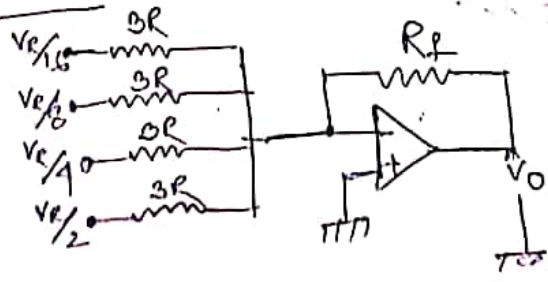the value of equivalent resistance $3R$ in each case,
 By superposition we can get the final equivalent
 circuit as,




$$S_0, V_0 = -R_f/3R \left(A_3 \cdot \frac{V_R}{2} + A_2 \cdot \frac{V_R}{4} + A_1 \cdot \frac{V_R}{8} + A_0 \cdot \frac{V_R}{16} \right)$$

$$V_0 = -\frac{R_f}{3R} \cdot \frac{V_R}{2^4} \left(2^3 A_3 + 2^2 A_2 + 2^1 A_1 + 2^0 A_0 \right)$$

• Resolution: In 4 bit converter, the smallest change in the o/p voltage i.e. resolution is given by,

$$\frac{\text{Full scale voltage}}{\text{Number of steps}} = \frac{R_f}{3R} \cdot \frac{V_R}{2^4} = V_R \cdot \frac{R_f}{48R}$$

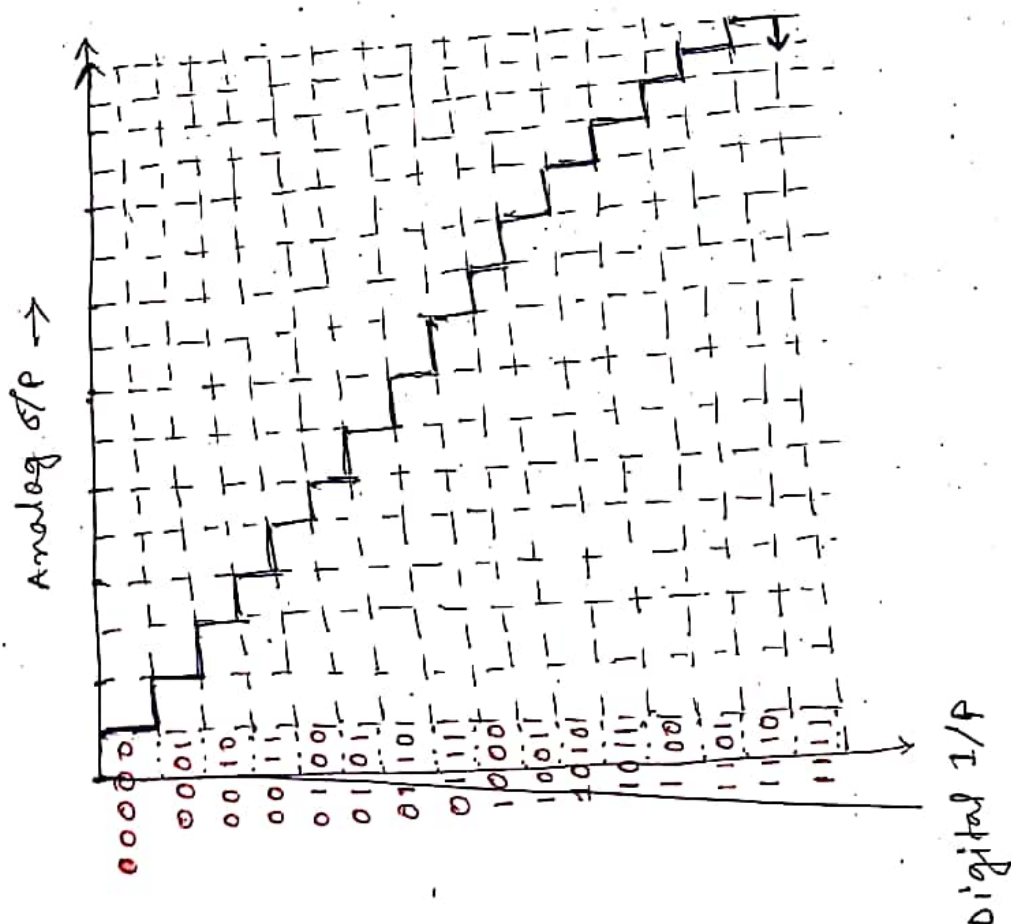with $V_R = 5V$, $R_f = 3R$, the voltage resolution is the order of $0.3V$. In 4 bit D/A, binary digits varied from 0000 to 1111 (0 to 15) and the output of the converter will assume a staircase waveform with 2ⁿ or 15 discrete steps.




• REST PART OF UNIT - I


• Problems will be uploaded shortly

Reference : B. Ghosh (Electronics)
Mehta-Mehta

CMRR:

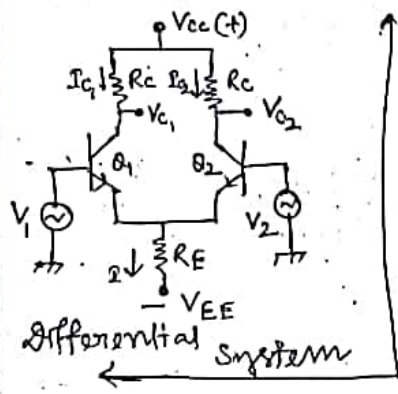

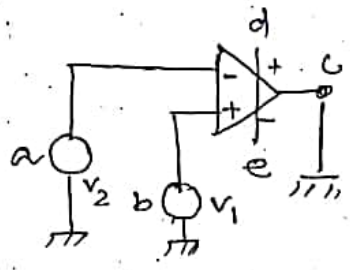An OPAMP is basically a differential amplifier with signal voltages v_1 and v_2 , each measured w.r.t. to ground.
 $v_1 \rightarrow$ to non-inverting terminal b
 $v_2 \rightarrow$ - inverting terminal a
 \rightarrow The o/p voltage v_o measured at 'c' w.r.t. to gnd.



In practice difference mode signal $v_d = v_1 - v_2$ and also average signal called common mode signal $v_c = \frac{v_1 + v_2}{2}$ are applied

to produce the o/p voltages. So,

$$\underline{\underline{So,}} \quad \boxed{v_o = A_1 v_1 + A_2 v_2}$$

$A_1 =$ voltage gain when 'a' is grounded
 $A_2 =$ " " " " " 'b' "

$$\underline{\underline{So,}} \quad v_1 = v_c + \frac{1}{2} v_d$$

$$v_2 = v_c - \frac{1}{2} v_d$$

$$v_o = \frac{1}{2} (A_1 - A_2) v_d + (A_1 + A_2) v_c$$

$$= A_d v_d + A_c v_c$$

$$\underline{\underline{So,}} \quad A_d = \frac{1}{2} (A_1 - A_2) \quad \left| \quad A_d = \text{voltage gain for difference signal.} \right.$$

$$A_c = \frac{A_1 + A_2}{2} \quad \left| \quad A_c = \text{voltage gain for common signal.} \right.$$

So, C.M.R.R i.e. Common mode Rejection Ratio.


$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{\frac{1}{2} (A_1 - A_2)}{A_1 + A_2} = \frac{A_1 - A_2}{2(A_1 + A_2)}$$

$$\bullet \quad CMRR = 20 \log_{10} \left| \frac{A_d}{A_c} \right| \text{ in dB}$$

A_d needs to be large and A_c needs to be small. The

amplifier design should be such that the C.M.R.R. is much larger than unity. * CMRR is to be infinitely large.

Slew Rate (SR)

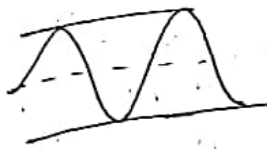


Slew rate of an OPAMP is a measure of how fast the output voltage can change and is measured in volts/μs.

— If S.R. of the OPAMP is 0.5 V/μs, it means that the OP from the amplifiers can change by 0.5V every μs. Since frequency is a function of time, the slew rate can be used to determine the maximum operating frequency of the OPAMP.

• Maximum operating frequency, $f_{max} = \frac{\text{Slew Rate}}{2\pi V_{pk}}$

$V_{pk} \rightarrow$ peak to peak o/p voltage.

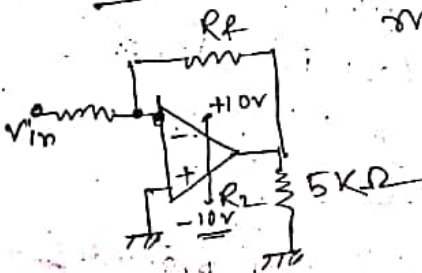• Determine Maximum operating frequency of the circuit, when, S.R = 0.5 V/μs : (Experimentally maximum peak to peak voltage $\approx 8V$)



So, $f_{max} = \frac{S.R.}{2\pi V_{pp}} = \frac{0.5 V/\mu s}{2\pi \times 8}$

or $0.5 V/\mu s = 500 KHz$

$\approx 9.95 KHz$

is not seen to be very high o/p frequency, then the amplifier must would be operating at its maximum o/p voltage.


• $8V_{as}$, $+V_{sat} = +V_{supply} - 2 = 10 - 2 = 8V$

• Now, if V_{pp} is small $\approx 100mV = 0.1V$.

$f_{max} = \frac{0.5 V/\mu s}{2\pi \times 0.1} = \frac{500 KHz}{2\pi \times 0.1} = 796 KHz$

So, the OPAMP is to be operated at much higher frequency thus when being used small signal amplifier than when being used as a large signal amplifier.

Frequency Response of an OPAMP

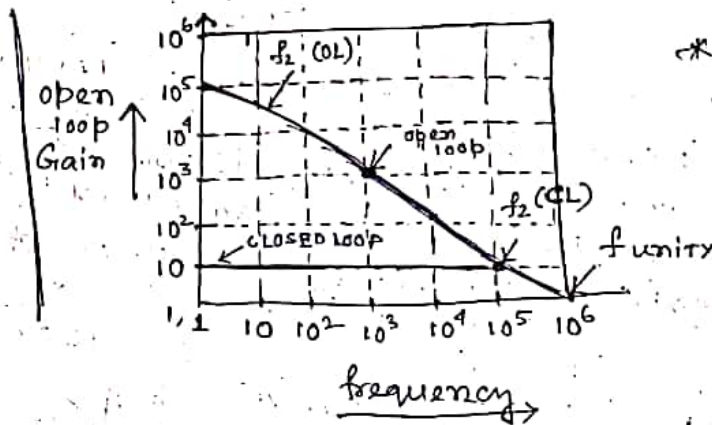

* frequency response of typical OPAMP IC $\mu A 741$

As a feedback amplifier of several stages an OPAMP can show gain instability, for this some commercial OPAMP are internally compensated for stability. The internal compensating capacitor makes the open loop bandwidth or upper cut off frequency $[f_2(OL)]$ i.e. the freq. at which the gain drops to $\frac{1}{\sqrt{2}}$ of the d.c. gain, very low. Lower cut off freq. is '0' here. for $\mu A 741$ the cutoff $f_2(OL)$ is order of 10 Hz. So, open loop OPAMP is not suitable for linear applications (a)

For ideal OPAMP, B.W. is practically infinite, but practically OPAMP under open loop configuration B.W. is low, of 10 Hz order only. So the OPAMP considered under closed loop configure, when the gain is somewhat low.

... When negative feedback is used overall B.W. increases, smaller is the closed loop gain (A_{CL}) used, the higher is the upper cut frequency $f_2(CL)$. However product $A_{CL} f_2(CL)$ is constant and is equal to open-loop unity gain frequency (f_{unity}). This product is known as Gain Band Width product (GBW)

when it is calculated for unit gain, the quantity is called unit gain Bandwidth (UGB).

⊗ General OPAMP. under that operation $S.R = 0.5 \text{ V/}\mu\text{s}$

• • Characteristics of the Frequency Response :

i) Maximum operating frequency of an OPAMP is given by $f_{\text{max}} = \frac{S.R.}{2\pi V_{\text{PP}}}$

• peak output voltage limits the maximum operating frequency.

ii) When the maximum operating frequency of an OP-AMP is exceed, the result is a distorted output wave form.

iii) Increasing the operating frequency of an OP-AMP beyond certain point —

- Decrease the maximum output voltage swing.
- Decrease the open loop voltage gain.
- Decrease the input impedance.
- increase the output impedance.