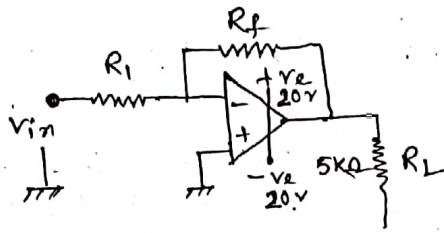


Q. Determine the maximum operating frequency for the circuit diagram. The slew rate is  $0.5 \text{ V}/\mu\text{s}$ ,  $V_{PP} = 16 \text{ V}$  (Given). [peak to peak] (CU 2000)




Ans: As the maximum output voltage ( $V_{PP}$ ) = ~~8V~~ 16V  
So, therefore maximum operating frequency ( $f_{max}$ )

$$f_{max} = \frac{\text{Slew Rate}}{2\pi V_{P-K}} = \frac{0.5 \text{ V}/\mu\text{s}}{2\pi \times 8} = \frac{500 \text{ kHz}}{2\pi \times 8} = 9.95 \text{ kHz}$$

$V_{P-K} = \frac{V_{PP}}{2}$


Q. For Given OPAMP configuration...

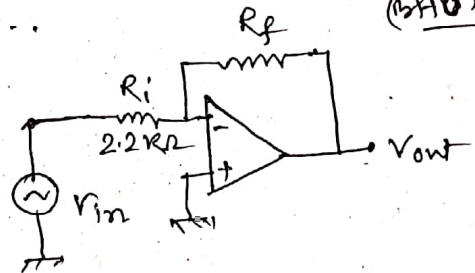2. Determine the value of  $R_f$  required to produce a closed loop voltage gain of -100



Ans!  $A_{CL} = -\frac{R_f}{R_i} \Rightarrow -100 = -\frac{R_f}{2.2}$   
 $R_f = 100 \times 2.2 \text{ k}\Omega = 220 \text{ k}\Omega$

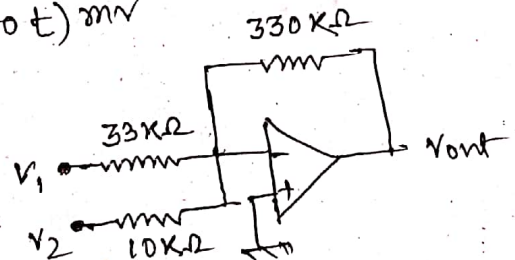Q. Calculate the output voltage for the circuit diagram. The inputs are  $V_1 = 50 \sin(1000t) \text{ mV}$ ,  $V_2 = 10 \sin(3000t) \text{ mV}$ . (CU 2000)




Ans: The o/p voltage of the circuit —

$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

$$= -\left[10V_1 + 33V_2\right] = -\left[10 \times 50 \sin(1000t) + \frac{33 \times 10}{1000} \sin(3000t)\right] \text{ mV}$$
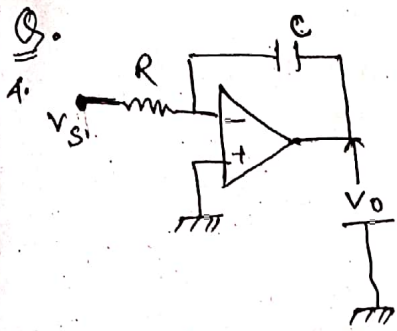
$$= -\left[0.5 \sin(1000t) + 0.33 \sin(3000t)\right] \text{ V}$$



Suppose a sinusoidal signal  $V_s = 10 \sin 2000\pi t$  mV is applied to the input of the OPAMP integrator  $R = 1\text{M}\Omega$  and  $C = 1\mu\text{F}$ . Find the output voltage? (DU)


Ans!

$$V_o = -\frac{1}{RC} \int_0^t V_s dt = \frac{1}{(1\mu\text{F})(1\text{M}\Omega)} \int_0^t 10 \sin 2000\pi t dt \text{ mV}$$

$$= -0.10 \left[ -\frac{\cos 2000\pi t}{2000\pi} \right]_0^t \text{ mV}$$

$$= \frac{1}{200\pi} [\cos 2000\pi t - 1] \text{ mV}$$

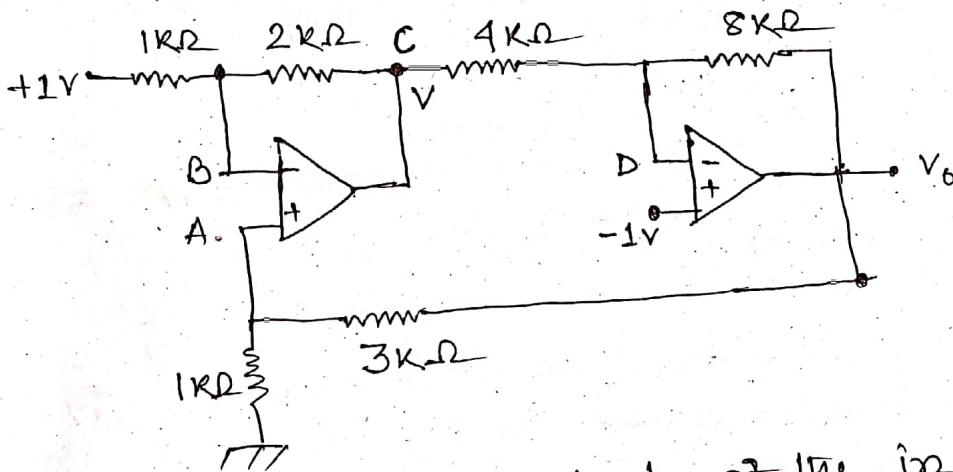Find the output voltage  $V_o$  in the circuit. (Gate)



Ans: Due to the virtual short at the input of the OPAMP we must have,

- $V_B = V_A = \frac{V_o \times 1}{1+3} = \frac{V_o}{4}$

- $V_D = -1\text{V}$

So, let the voltage at C be  $V$

Now Assuming infinite input impedance of the OPAMPs, we can say that almost same current passes through the resistor  $1\text{k}\Omega$  and  $2\text{k}\Omega$

So,

$$\frac{1 - V_B}{1k\Omega} = \frac{V_B - V}{2k\Omega} \Rightarrow$$

$$\frac{1 - V_0/4}{1} = \frac{V_0/4 - V}{2} \quad \text{--- (1)}$$


Similarly,  $\frac{V - V_D}{4} = \frac{V_D - V_0}{8} \Rightarrow$

$$\frac{V+1}{4} = \frac{-1 - V_0}{8} \quad \text{--- (2)}$$

from solving above two eqn we get  $V_0 = 0.4V$

Q  
6.

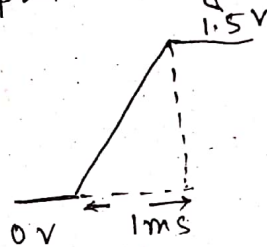A ramp voltage of  $1.5V/ms$  is applied to an OP-AMP differentiator with  $R = 2k\Omega$  and  $C = 0.01\mu F$ . Find the output voltage and its waveform.



Ans: From figure,  $\frac{dV_s}{dt} = 1.5V/ms$ , within the 1ms range  
 $= 0$ ; outside the 1ms range.

Now, the output,

$$V_0 = -RC \frac{dV_s}{dt}$$


$$= - (0.01\mu F) (2k\Omega) \times 1.5V/ms$$

$$= -0.03V$$


$$= -30mV \text{ within the 1ms range.}$$

and,  $V_0 = 0$ , without 1ms range.

Thus the resultant waveform,

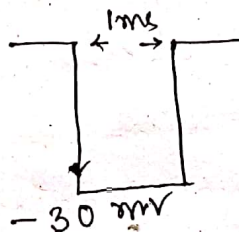

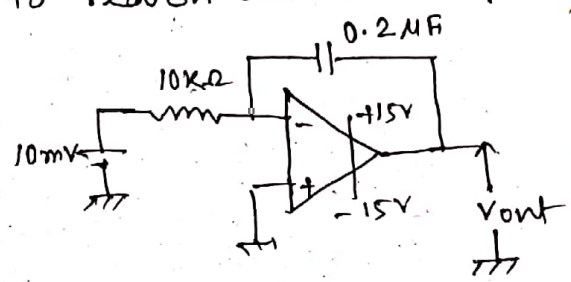Q. 7. For the integrator circuit. How long it take for the output to reach saturation? (DU 09)




Soln : Output voltage,  $V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$   
 As, the input voltage  $V_{in} (= 10mV)$  is constant

$$V_{out} = -5t \text{ volts}$$

Now, the theoretical saturation voltage is 15V as it is the negative supply

$$V_s = -15V$$

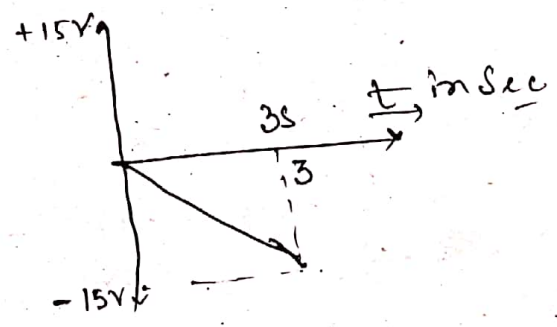
So,  $V_s = V_{out}$   
 $-15 = -5t$   
 $t = 3s$



Assignment: 5x4=20Mark

1. Find the output voltage for the circuit? (and output wave from also drawn)


(IISC'02)

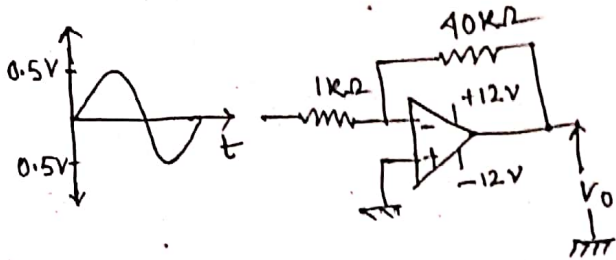

$V_o = ?$

④

2.

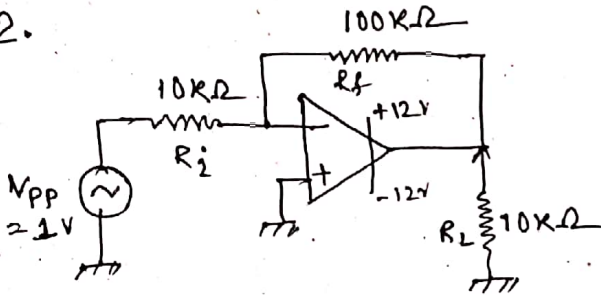

For the circuit.

- i) What is the closed loop gain?
- ii) Input impedance of the circuit?
- iii) the maximum operating frequency when slew rate is 0.5 V/μs.


frequency when slew rate is 0.5 V/μs.

④

3.

Determine the output voltage from the circuit for each of the following input combinations.

④

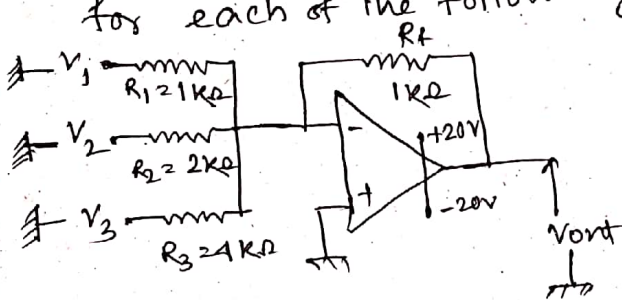


$V_1 (V)$	$V_2 (V)$	$V_3 (V)$
+10	0	+10
0	+10	+10
+10	+10	+10

4.

For the OPAMP integrator and the square wave input. Find the output voltage (draw wave from output)

④

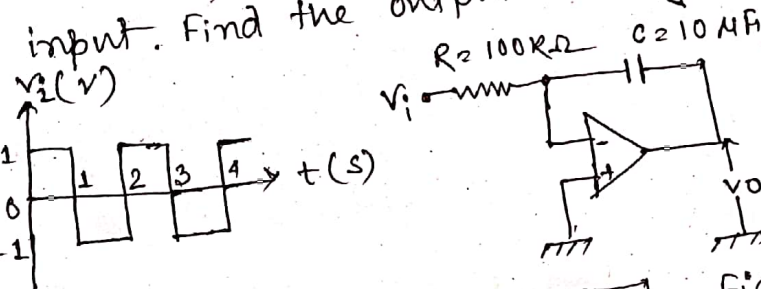

[CU Entrance Test]

5.

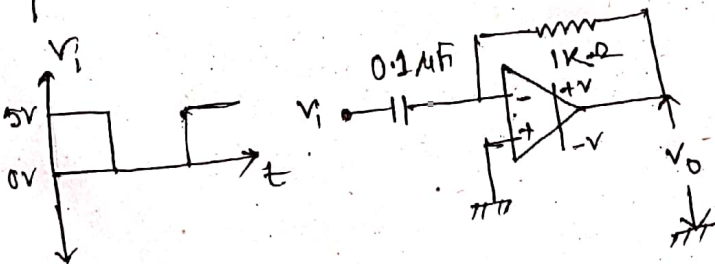


Figure shows the square wave input to a differentiator circuit. Find the output voltage if input goes from 0V to 5V in 0.1ms.

[RAT]